

Quiz 18

$$1) a) I_{cm} = \frac{P_{cm}}{V} = \frac{1200W}{120V} = 10A$$

$$P_{cm} = 1200 \text{ Watts}$$

$$P_+ = 1100 \text{ Watts}$$

$$P_{WI} = 1400 \text{ Watts}$$

$$I_+ = \frac{P_+}{V} = \frac{1100W}{120V} = 9.17A$$

$$I_{WI} = \frac{P_{WI}}{V} = \frac{1400W}{120V} = 11.67A$$

$$b) I_{total} = I_{cm} + I_+ + I_{WI} = 10A + 9.17A + 11.67A = 30.84A$$

c) Yes a 35-A circuit breaker is sufficient since the total current is less than 35A so there won't be a problem when all devices are on.

$$2) R_1 = ? \quad R_2 = ?$$

$$\text{in series} \quad R_{eq} = R_1 + R_2 \Rightarrow 690\Omega = R_1 + R_2, \quad R_1 = 690\Omega - R_2$$

$$\text{in parallel} \quad \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow \frac{1}{150\Omega} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow \frac{R_1 + R_2}{R_1 R_2}$$

$$\Rightarrow R_1 + R_2 = \frac{R_1 R_2}{150\Omega} \quad \Rightarrow$$

$$(690\Omega - R_2) + R_2 = \frac{(690 - R_2) R_2}{150\Omega}$$

$$690\Omega = \frac{690\Omega R_2 - R_2^2}{150\Omega} \Rightarrow 103,500\Omega = 690R_2 - R_2^2$$

$$\Rightarrow R_2^2 - 690R_2 + 103,500\Omega = 0$$

$$x = \frac{-(-690) \pm \sqrt{(-690)^2 - 4(1)(103,500)}}{2(1)} \quad + = 469.59\Omega$$

$$R_2 = 220.4\Omega$$

$$220.4 + R_1 = 690\Omega$$

$$R_1 = 469.6\Omega \quad R_2 = 220.4\Omega$$

$$R_1 = 469.6\Omega$$