

1) A piece of Nichrome wire has a radius of $6.5 \times 10^{-4} \text{ m}$, it is used in a lab to make a heater that uses 400 W of power when connected to a voltage source of 120 V . Ignoring the effect of temp on resistance, determine the necessary length of the wire.

$$P = 400 \text{ W} \quad V = 120 \text{ V} \quad P = IV \quad r = 6.5 \times 10^{-4} \text{ m}$$

$$I = \frac{P}{V} = \frac{400 \text{ W}}{120 \text{ V}} = 3.33 \text{ A} \quad \text{resistivity} = 1.00065 \text{ m} \rightarrow \rho = 1.0 \times 10^{-6} \text{ m}$$

$$A = \pi r^2 = \pi (6.5 \times 10^{-4})^2 = 1.3 \times 10^{-6} \text{ m}^2$$

$$R = \frac{V}{I} = \frac{120 \text{ V}}{3.3 \text{ A}} = 36.36 \Omega$$

$$R = \frac{\rho L}{A} \Rightarrow L = \frac{AR}{\rho} = \frac{(1.3 \times 10^{-6} \text{ m}^2)(36.36 \Omega)}{1.0 \times 10^{-6} \text{ m}}$$

$$= 47.19 \text{ m}$$

2) Voltage Rule -

The algebraic sum of all potential drops/increases across a closed loop circuit is zero.

conservation of energy

$$\Delta U = 0 \text{ J}$$

2) $15\text{-}\Omega$ toaster is turned on in a circuit which already has a .2 hp motor, three 100-W light bulbs and a 600 W electric iron that are on, will this trip a 15-A circuit breaker?

$$I_1 = \frac{V}{R} = \frac{120\text{ V}}{15\Omega} = 8\text{ A}$$

$$P = IV \Rightarrow I_2 = \frac{P}{V} = \frac{149.2\text{ W}}{120\text{ V}} = 1.24\text{ A}$$

$$I_3 = \frac{P}{V} = \frac{3(100\text{ W})}{120\text{ V}} = 2.5\text{ A}$$

$$I_4 = \frac{P}{V} = \frac{600\text{ W}}{120\text{ V}} = 5\text{ A}$$

$$I = 8\text{ A} + 1.24\text{ A} + 2.5\text{ A} + 5\text{ A} = 16.74\text{ A}$$

This will trip the circuit since $16.74\text{ A} > 15\text{ A}$.